

OTHER ST PRODUCTS TO CHECK

| | | |
|--|---|--|
| ADC120 | ISOSD61 | STISO621 |
| 12-bit ADC converter 8 channels Speed 50ksps to 1Msp ENOB 11.7 bits | 16-bit isolated Sigma-Delta modulator Input range ±320mV Output 25Msp 1-bit stream | Digital isolator Dual channel for UART Up to 100Mbps |

GLOSSARY

Bidirectional – Ability of the device to measure current in both negative and positive directions.

Unidirectional – Unidirectional current sensing measures current in one direction only. The opposing direction is sensed as zero.

Output common mode – Shift of the output voltage by a certain Vref in order to allow bidirectional measurement. When using op amps, a small output common mode also prevents output from entering saturation and therefore provides better response to small currents.

Input Common mode voltage – Common voltage which is applied to both inputs of the circuit. This voltage is not part of the useful signal and should not be amplified.

Common mode rejection ratio (CMRR) – Measure of a device's ability to filter out the common mode voltage. This is important for high-side or in-line current sensing.

H-bridge – Transistors connected in such a way as to control voltage and its polarity applied to the load.

Gain bandwidth product (GBP) – Product of the gain and maximum small signal frequency. A circuit able to amplify 10kHz with 40dB gain has the same GBP as a circuit amplifying 100kHz with 20dB gain. This parameter is specified in op amp datasheet.

Bandwidth (BW) – Signal frequency at which the amplitude drops by 3dB. This is specified in datasheets for current sense monitors.

Input offset voltage (Vio) – Differential input voltage of the In+ and In- pins to obtain the output at the mid-range of the supply voltage. It originates from the matching of internal transistors.

Input offset voltage drift (dVio/dT) – Drift of the input offset voltage with temperature. This might be important for motor control applications.

Input bias current (Iib) – Current flowing through device inputs. Due to device biasing requirements and normal operation leakage, a very small amount of current (pA or nA range, depending on the technology) flows through its inputs.

Zero drift – Technology designed to self-correct device parameters by compensating Vio errors and those occurring with temperature and with time. Zero drift or chopper devices have their Vio in the order of microvolts and nanovolts per Celsius degrees drift. Zero drift virtually cancels 1/f noise and mitigates aging over time.

Rail-to-rail input – An op amp with a high-rail input can work with input signals up to Vcc+, while a low-rail input is able to deal with signals down to Vcc-. Rail-to-rail input op amps can handle input signals from Vcc- to Vcc+.

EMI filter – filter to suppress the impact of electromagnetic interferences. As current sensors are always connected to external wires, some external sources may produce EMI disturbance. Current sense monitors and some high-performance op amps usually feature embedded EMI filters.

For more information, visit us on www.st.com/current-sense-amplifiers and www.st.com/opamps

life.augmented

Current Sensing Quick reference guide



For more information on ST products and solutions, visit www.st.com

© STMicroelectronics - November 2021 - Printed in United Kingdom - All rights reserved
ST and the ST logo are registered and/or unregistered trademarks of STMicroelectronics International NV or its affiliates in the EU and/or elsewhere. In particular, ST and the ST logo are Registered in the US Patent and Trademark Office.
For additional information about ST trademarks, please refer to www.st.com/trademarks.
All other product or service names are the property of their respective owners.


life.augmented



Order code: BRCSENSINGQR1121



Current sensing is important in many industrial and automotive applications like motor control, battery management, power management, and many others. ST provides solutions for these applications based on [operational amplifiers](#) and integrated current monitors for shunt current sensing.

HOW DOES IT WORK ?

Our current sensing solution involves a shunt resistor and the straightforward application of Ohm's law. A tiny resistance is placed on the current path and the linear voltage drop is amplified to derive a precise current measurement.

All resistors dissipate power in the form of heat, and this unwanted effect is also present to some extent in shunt resistors. While a lower shunt resistance will minimize the impact, the drawback is that higher amplification gain will be required, which lowers overall measurement precision.


POSITION OF THE SHUNT

Shunt resistors can be placed in several different locations to measure current through an application. Each of them has certain advantages and disadvantages.

High-side – Shunt resistor is placed on the power rail. In this case, the current sensor is directly on the supply voltage, so its maximum input common mode voltage needs to be high enough to manage the supply voltage. High-side shunt resistors are used in applications where ground cannot be cut for mechanical reasons, RF disturbances, or other currents flowing to ground.

In-line – Also called phase current sensing. Shunt resistors can be placed in line with motors in motor control applications, but this requires bidirectional current sense monitoring. While it offers the advantage of tracking current all the time, fast voltage transients will be present due to the switching activity of the H bridge, and the device must be able to recover quickly after such common mode voltage shifts.

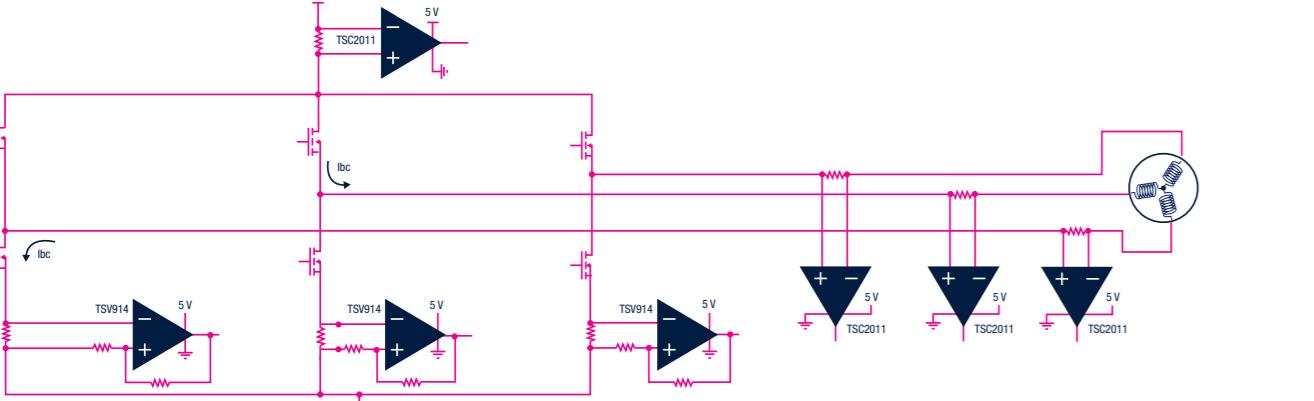Low side – In this case, the shunt is place on the ground line, so the common mode voltage is close to 0V, and low voltage technology is sufficient. This is a popular solution because simpler and cheaper op amps can be employed.



SHUNT RESISTOR VALUE AND SIZE

Shunt value selection involves balancing dynamic range and power dissipation. Lower shunt values inflict smaller losses, but higher amplification gain is needed, and devices having a certain gain bandwidth product (GBP) incur a slower response dealing with higher gains.

The precision of current amplifiers have a large impact on final shunt values and power dissipation. High precision devices can work with higher gain to maintain the same output accuracy as standard components, while allowing smaller shunt values.

To calculate critical shunt values and sizes, the total current range must be known. While the range is simply the maximum current for unidirectional measurement, the maximum currents in each direction must be summed for bidirectional readings. Given the current range, along with the maximum output voltage and gain, the following equations provide the maximum value of the shunt and its power dissipation.

$$R_{\text{sense}} \leq \frac{V_{\text{outMax}}}{I_{\text{range}} \cdot \text{Gain}}$$

$$P_{\text{Max}} \geq R_{\text{sense}} \cdot I_{\text{max}}^2$$

The final shunt value should always be smaller than the theoretical value to account for imperfections and errors. A smaller shunt value also gives some margin to measure overcurrent and prevent saturation. The maximum power dissipation of the shunt resistor must be higher than the calculated value.

ST PRODUCT AND PORTFOLIO

| Unidirectional current monitors | TSC101A TSC101B TSC101C | TSC88A TSC88B TSC88C | TSC102 TSSOP8 S08 Operating 2.8 to 30V Gain x20 adj. | TSC103 TSSOP8 S08 Operating 2.9 to 70V AMR -16 to 75V Gain x50 x100 |
|---------------------------------|--|--|---|---|
| | SOT23-5 Operating 2.8 to 30V Gain x20 x50 x100 | SOT23-5 Operating 2.8 to 24V Gain x20 x50 x100 | | |

| Bidirectional current monitors | TSC2010 TSC2011 TSC2012 | TSC210 TSC211 TSC212 | TSC214 TSC215 | TSC213 |
|--------------------------------|--|---|--|---|
| | MiniS08 S08 Operating -20 to 70V Bandwidth 600kHz Gain x20 x60 x100 | SC70-6 QFN10 Operating -0.3 to 26V Gain x200 x500 x1000 Vio max 35µV | SC70-6 QFN10 Operating -0.3 to 26V Gain x100 x75 Vio max 60µV | SC70-6 QFN10 Operating -0.3 to 26V Gain x50 Bandwidth 100kHz Vio max 100µV |



| Operational amplifiers | TSV7721 TSV7722 | TSV791 TSV792 | TSZ181 TSZ182 | TSB7191A TSB7192A |
|------------------------|---|---|---|---|
| | Single / dual Operating 1.8 to 5.5V Low rail only input Vio max 200µV GBP typ 22MHz | Single / dual Operating 2.2 to 5.5V Vio max 200µV (44µV) GBP typ 50MHz | Single / dual Operating 2.2 to 5.5V Vio max 35µV (44µV) GBP typ 3MHz | Single / dual Operating 2.7 to 36V Vio max 300µV GBP typ 22MHz |

Automotive-grade version available

Extended temperature range (-40 to +150°C) available

CURRENT SENSE MONITOR VS OPERATIONAL AMPLIFIER

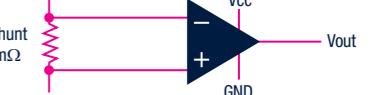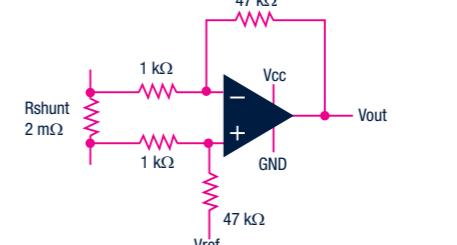In many applications with input common mode voltage below 30V, the choice between a current sense monitor or operational amplifier is a matter of designer preference, regardless of whether bidirectional or unidirectional current sensing is required. Current monitors must instead be used for applications with common mode voltages above the maximum operating voltages of op amps.



Operational amplifiers

- External components needed
- Common mode voltage limited to Vcc, or lower if device is not rail to rail
- More complex design
 - Additional filtering can be implemented
 - Any gain can be set
 - Actual bandwidth needs to be calculated
 - More difficult design / error calculations

Current sense monitors


- No external components needed (except shunt)
- Common mode usually higher than Vcc
- Simple design but performance cannot be adjusted
- Fully specified bandwidth, output errors and other parameters
- May provide additional integrated features (EMI filters, PWM rejection, comparator, Vref, etc.)

APPLICATIONS

Battery management systems



Low voltage motor control

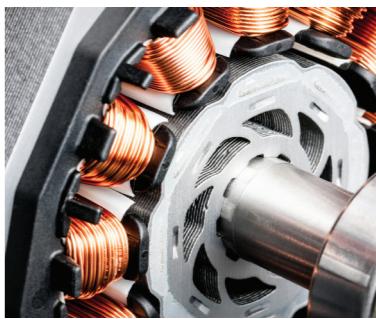

Power inverters



Battery management systems require bidirectional and very high precision current sensing to minimize energy losses. The sensing rate is usually low, and both high-side and low-side can be adopted. Isolated current sensing is not required up to 48V.

Driving a motor requires sufficient sensing rates for correct operation. Shunt power dissipation is negligible with respect to the consumption of the motor, so some energy losses can be sacrificed for faster sensing. Bidirectional in-line or unidirectional high-side current sensing is usually preferred.

ACDC and DCDC power inverters measure current at several places, based on the topology. Control loops usually implement low-side current sensing with op amps, while high-side current sense monitors are generally used for output power monitoring.